



Tanta University
Faculty of Engineering
Electrical Power and Machines Engineering
Department
Electrical machine 2..... 2014/2015



Sheet (3)

- 1) A single-phase, 300kVA, 11kV/2.2kV, 60Hz transformer has the following equivalent circuit parameters referred to the high-voltage side:

R_{cHV}	57.6k Ω
X_{mHV}	16.34k Ω
X_{eqHV}	8.45 Ω
R_{eqHV}	2.784 Ω

(a) Determine:

- (i) No-load current as a percentage of full-1 ϕ load current.
- (ii) No-load power loss (i.e., core loss).
- (iii) No-load power factor.
- (iv) Full-load copper loss.

(b) If the load impedance on the low-voltage side is $Z_{load} = 16 \angle 60^\circ \Omega$ determine the voltage regulation using the approximate equivalent circuit.

- 2) A 1 ϕ , 250 kVA, 11kV/2.2kV, 60Hz transformer has the following parameters.

$R_{HV} = 1.3 \Omega$	$X_{HV} = 4.5 \Omega$
$R_{LV} = 0.05 \Omega$	$X_{LV} = 0.16 \Omega$
$R_{cLV} = 2.4k\Omega$	$X_{mLV} = 0.8k\Omega$

(a) Draw the approximate equivalent circuit (i.e., magnetizing branch, with R_c and X_m connected to the supply terminals) referred to the HV side and show the parameter values.

(b) Determine the no-load current in amperes (HV side) as well as in per unit.

(c) If the low-voltage winding terminals are shorted, determine

- (i) The supply voltage required to pass rated current through the shorted winding.
- (ii) The losses in the transformer.

(d) The HV winding of the transformer is connected to the 11kV supply and a load, $Z_{load} = 15 \angle -90^\circ \Omega$ is connected to the low-voltage winding. Determine:

- (i) Load voltage.
- (ii) Voltage regulation

3) A1 ϕ , 25kVA, 2300=230V transformer has the following parameters:

$$\begin{array}{ll} Z_{eq.H} & 4.0 + j5.0\Omega \\ R_{c.L} & 450\Omega \\ X_{m.L} & 300\Omega \end{array}$$

The transformer is connected to a load whose power factor varies. Determine the worst-case voltage regulation for full-load output.

4) For the transformer in Problem3:

- (a) Determine efficiency when the transformer delivers full load at rated voltage and 0.85 power factor lagging.
- (b) Determine the percentage loading of the transformer at which the efficiency is a maximum and calculate this efficiency if the power factor is 0.85 and load voltage is 230V.

5) A1 ϕ , 10 kVA, 2400/240 V, 60 Hz distribution transformer has the following characteristics:

Core loss at full voltage=100W

Copper loss at half load=60W

- (a) Determine the efficiency of the transformer when it delivers full load at 0.8 power factor lagging.
- (b) Determine the per-unit rating at which the transformer efficiency is a maximum. Determine this efficiency if the load power factor is 0.9.
- (c) The transformer has the following load cycle:

No load for 6 hours

70% full load for 10 hours at 0.8 PF

90% full load for 8 hours at 0.9 PF

Determine the all-day efficiency of the transformer.

6) A 320-kVA, 240/4800-V, 60-Hz transformer yielded the following information when tested:

	Voltage(v)	Current(A)	Power(w)
--	------------	------------	----------

Open-circuit test	240	39.5	1200
Short-circuit test	195	66.67	3925

Find the equivalent circuit of the transformer as viewed from (a) the low-voltage side and (b) the high-voltage side.

- 7) A 5-kVA, 500/250-V, 50-Hz transformer yielded the following information when tested:

	Voltage(v)	Current(A)	Power(w)
Open-circuit test	500	1	50
Short-circuit test	25	10	60

- Determine the efficiency of the transformer when it delivers full load at 0.8 power factor lagging.
- Determine the voltage regulation of the transformer when it delivers full load at 0.8 power factor lagging.
- Determine the efficiency of the transformer when it delivers 60% full load at 0.8 power factor leading.
- Obtain an equivalent circuit of the transformer Referred to the high-voltage side.